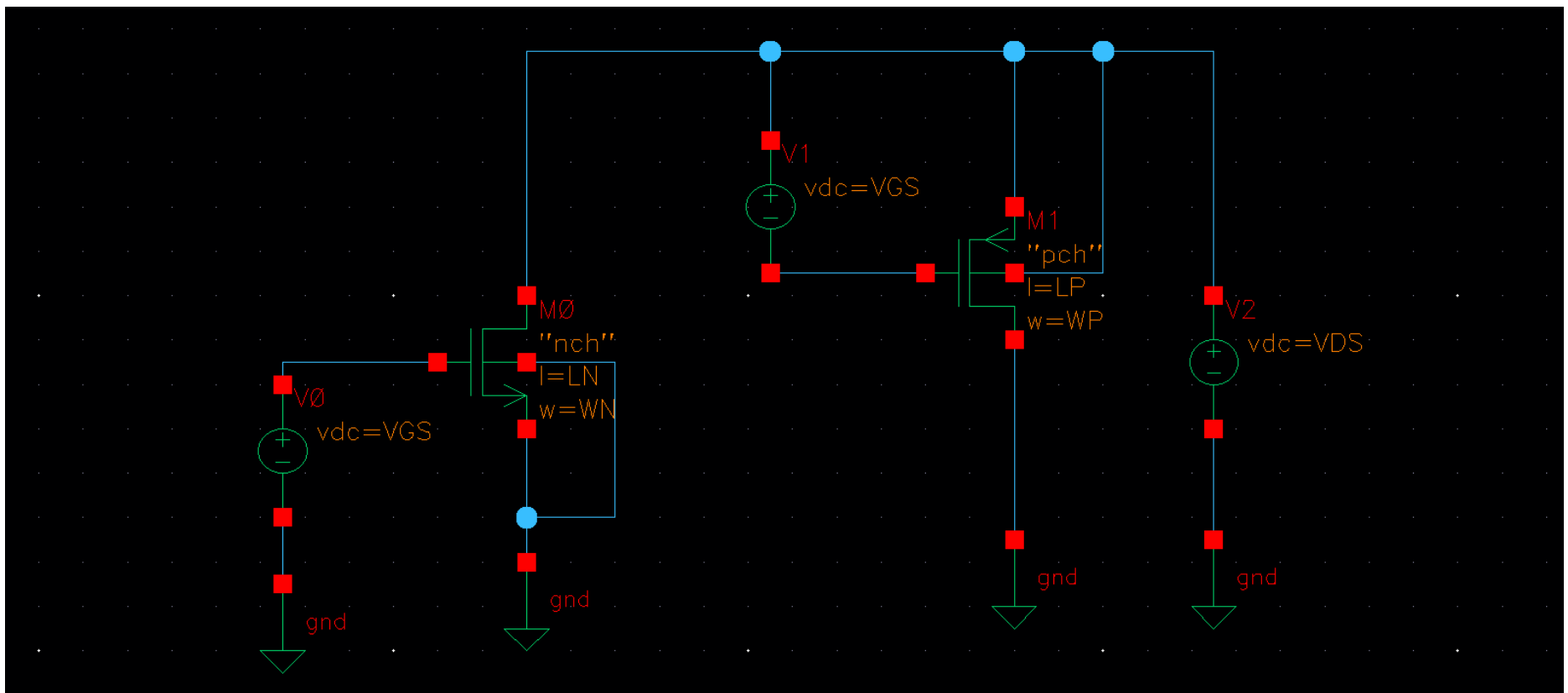


# LAB 2

## PART 1 (Sizing chart):


### Circuit:



### //comments:

- To design a resistive loaded CS amplifier that meets our specifications. The design process involves selecting the sizing of the transistor ( $W$  and  $L$ ), the bias point ( $VGS$ ), and the resistive load ( $RD$ ).
- A relatively long  $L$  is chosen to provide large  $r_o$  and avoid short channel effects.

## V\* plot:

 


## //comments:

First, a DC analysis is made and  $V_{GS}$  is swept from 0 to  $v_{th}+0.4(0.8)$  with a step size equal to 10m V.

$V^* = 2 \cdot I_D / g_m$ , so  $v^*$  is plotted by sending the  $I_D$  and  $g_m$  to the calculator to get their expressions then  $v^*$  equation is built.


## Vov plot:

 

## //comments:

$V_{ov} = V_{gs} - V_{th}$ , so  $V_{ov}$  is plotted by sending  $V_{gs}$  and  $V_{th}$  to that calculator to get their expressions, then  $V_{ov}$  is plotted.

 
**V\* and Vov plot (after modifying the Y-axis):**



//comments:

- The Y-axis constraints were modified to have the same range.
- From the plotting, it is clear that before the subthreshold operation as we go down the threshold value it is found that the deviation is large between the  $V^*$  &  $V_{ov}$ .
- And they are very close at the moderate values (moderate inversion) which is between subthreshold and under saturation.
- In saturation there is discrepancy as the device is still short channel, but this discrepancy is somehow acceptable.
- Generally, in real  $V_{Dsat}$  of a transistor the curve of  $V^*$  and  $V_{ov}$  will be closer than this.
- And, You will notice that at the beginning of the strong inversion region,  $V^*$  and  $V_{ov}$  are relatively close to each other (i.e., square-law is relatively valid). For deep strong inversion (large  $V_{ov}$ : velocity saturation and mobility degradation) or weak inversion (near-threshold and subthreshold operation) the behavior is quite far from the square-law (although we are using  $L = 2\mu m$ ).
- Since,  $V^*Q = 2V_{rd}/A_v$ ,  $V_{rd} = V_{dd}/2 \rightarrow$  Then,  $V^*Q = 2 \cdot 0.9/6 = 300m V$ .

 
## VgsQ and VovQ conclusion from the ( $V^*$ -Vov) plot:



//comments:

- Then,  $V_{gsQ} = 689\text{mV}$  &  $V_{ovQ} = 307\text{mV}$  &  $V^*Q = 300\text{mV}$  {calculated in the previous page}.
- Then, we get the values of  $I_d$ ,  $g_m$  and  $g_{ds}$  at the  $V_{gsQ}$  ( $689\text{mV}$ ) and will be named  $I_{Dx}$ ,  $g_{mx}$ , and  $g_{dsx}$  respectively.


## ID plot:

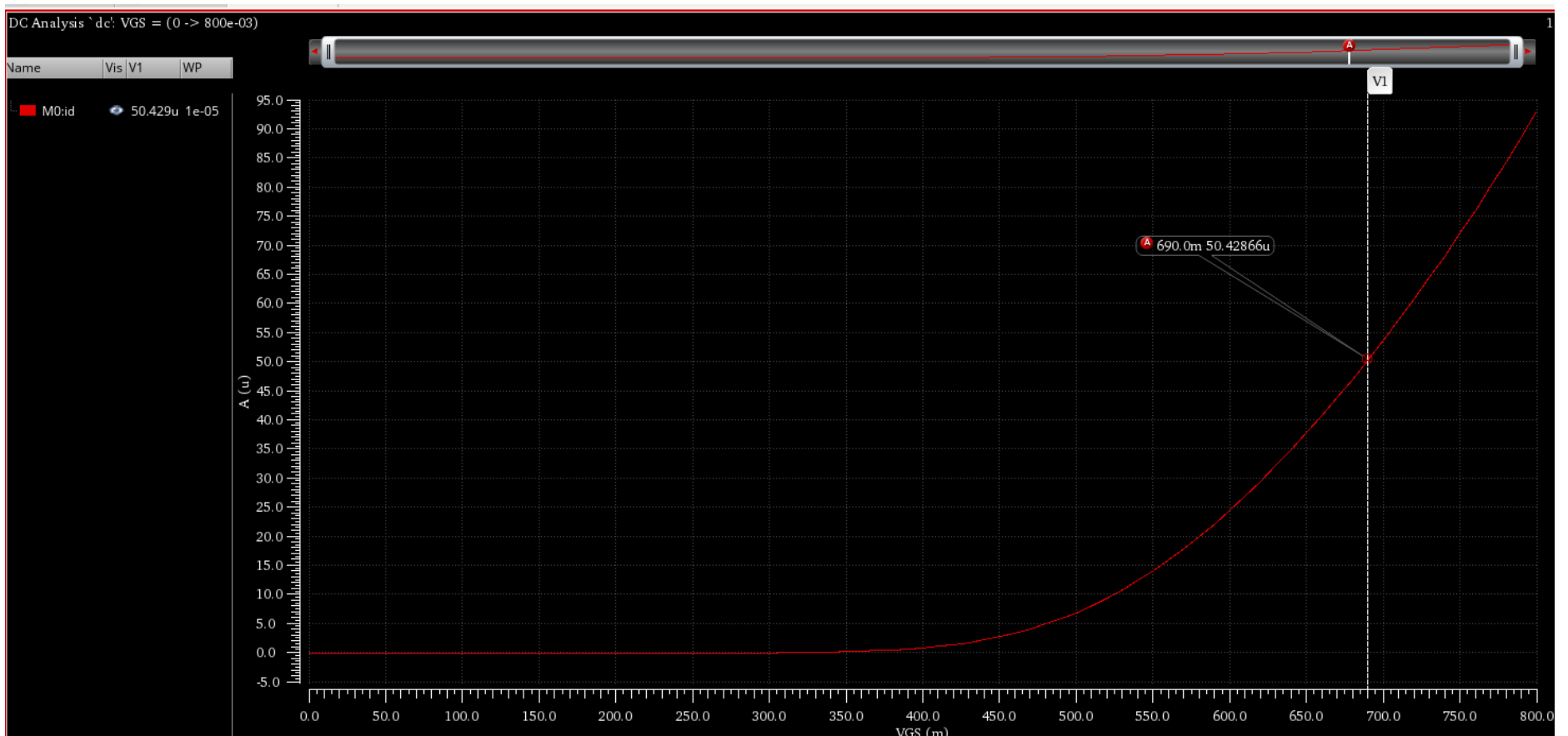

//comments:

- Then,  $I_{Dx} = 50.5\text{uA}$
- There is difference between required  $I_d$  and  $I_{Dx}$  due to linearity between device width and current, so a simple scaling is done to get the actual width *\_in the next pages*


gm plot:

 

//comments:

- Then,  $gm_x = 333.3536u$

gds plot:

 

//comments:

- Then,  $gds_x = 1.973707u$


//comments:

- Now back to the assumption that we made that  $W = 10\mu m$ . This is not the actual value that we will use for our design. But the good news is that  $ID$  is always proportional to  $W$  irrespective of the operating region and the model of the MOSFET (regardless square-law is valid or no). Thus, we can use ratio and proportion (cross-multiplication) to determine the correct width at which the current will be  $IDQ = 150\mu A$  as given in the specs So we Calculate  $W$  as shown below.
- Then actual width = 29.7u
- And by using the cross-multiplication method again we get:
  - $gm_q = 992.12u$
  - $gds_q = 5.874u$
  - $ro_q = 1/gds_q = 1.7 \cdot 10^5 \Omega$
- Then,  $Av = -gm(RD || ro)$  meet the required gain spec.

## PART 2 (CS amplifier):

### 1<sup>st</sup>: OP & AC analysis


circuit:

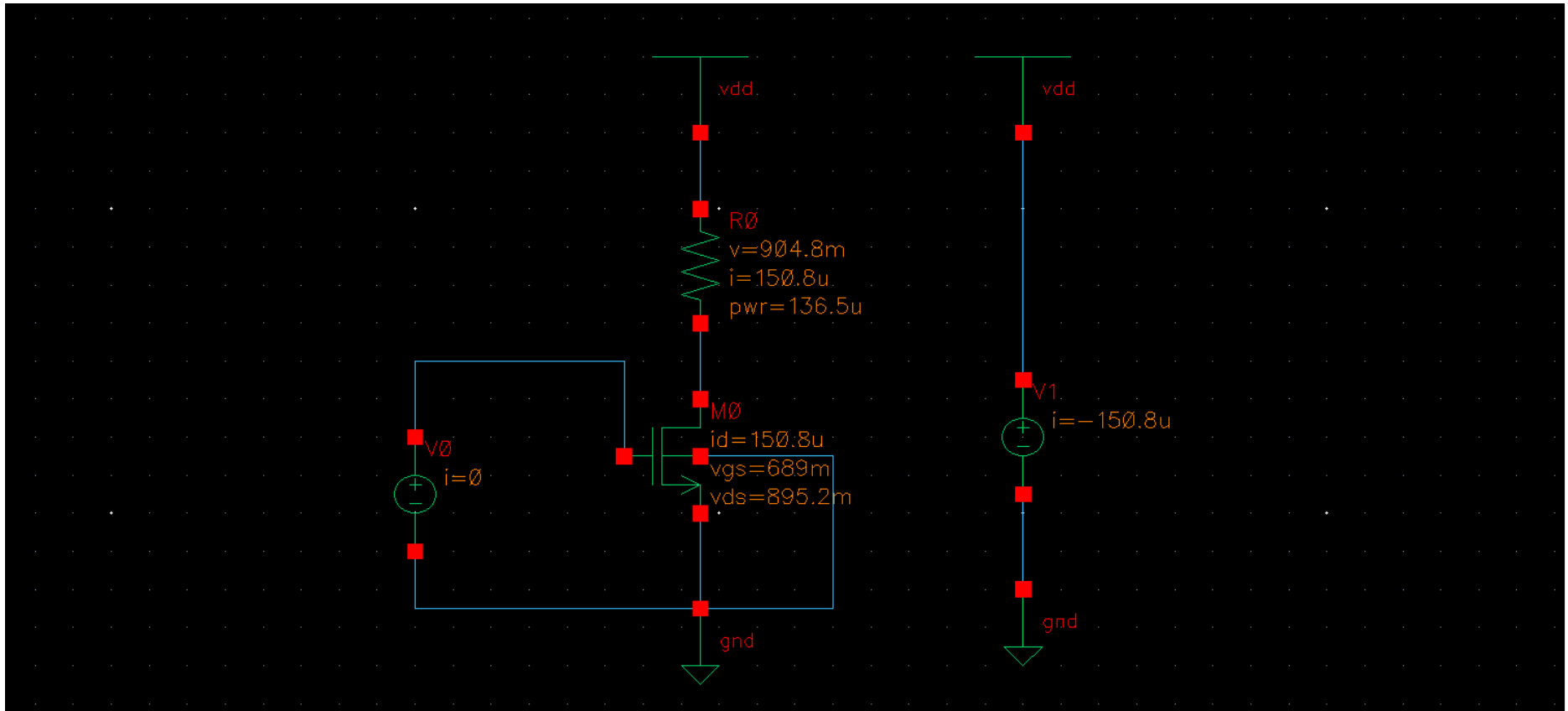

//comments:

- A testbench is created for the resistive loaded amplifier using VgsQ, Rd, L and W that we get from the previous part.
- Since  $R_d = V_{rd}/I_d$  then  $R_d = 6k\ \Omega$  *\_other variables are calculated before*

DC OP:

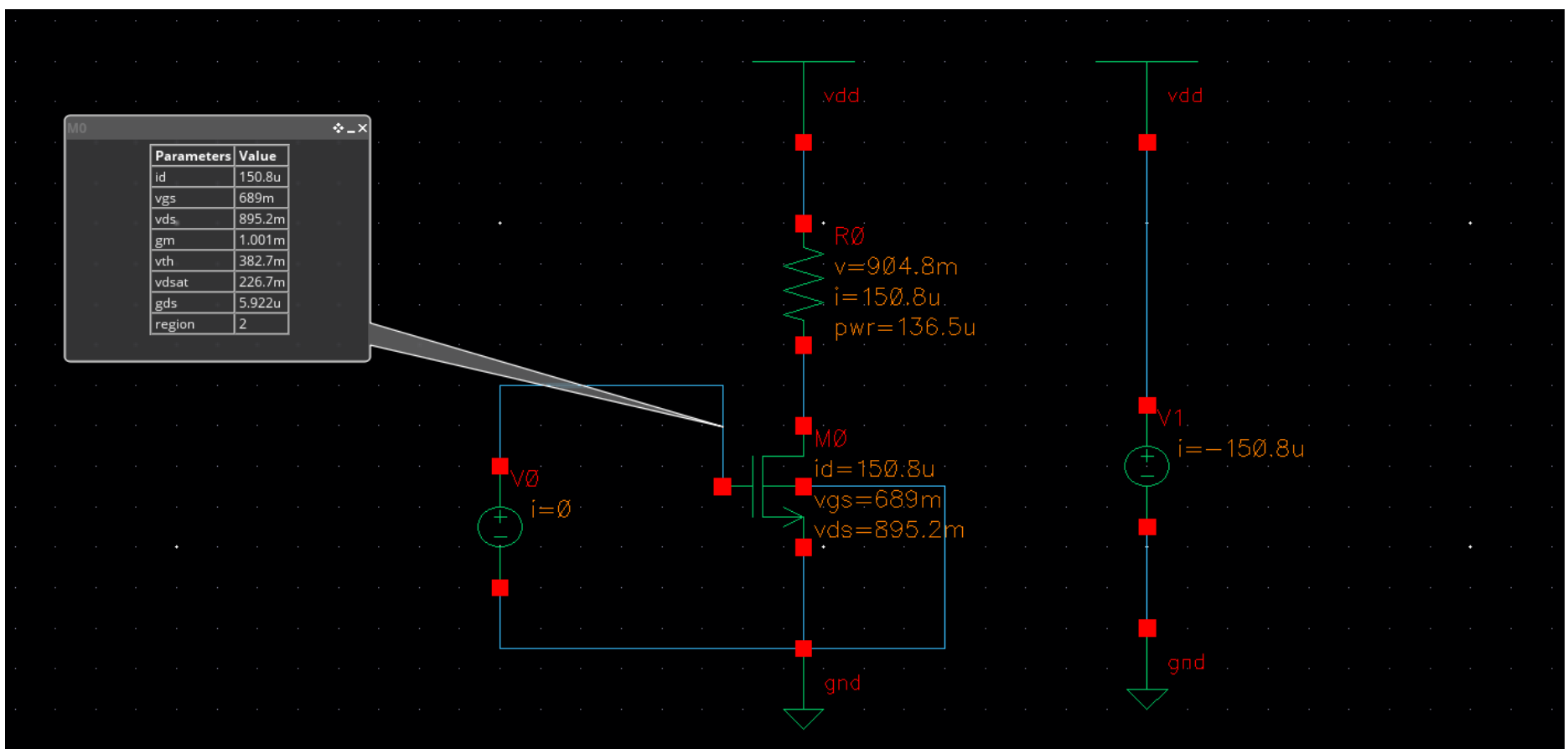

//comments:

- Results are pretty similar to that we used before in chart-based design.



*//follow comments on DC OP results:*

- Since that we got  $V_{Dsat} = 226.7\text{m V}$  and  $V^* = 300\text{m V}$ , Then this shows how the  $V^*$  put a safety margin on the expected value of the  $V_{Dsat}$ .
- Since  $g_m$  scale is linear with Width, then  $g_m$  of new device almost have the same scale of the old one.
- $G_{ds}$  scale decreases with the same factor the  $i_d$  scale increases with.
- Then, the design is almost on point.

*//comments:*

- Since  $r_o = 1/g_{ds} \approx 1/6\mu \approx 166.6\text{k } \Omega$ , Then very large value in the Q range
- Then  $r_o \gg R_d$  ( $6\text{k } \Omega$ ), Then approximation is justified and assumption of ignoring  $r_o$  is justified and error value is not to be considered.
- If we used min L  $\rightarrow$  the assumption will not be justified as when L decreases, then the output resistance decreases.


*//comments:*

- Intrinsic gain is when CS device is loaded with current source or loaded in AC with open load (NO load).
- Intrinsic gain =  $g_m/g_{ds} = 1\text{m}/6\mu = 166.6$
- Intrinsic gain is the highest gain I can reach.

*//comments:*

- Amplifier gain  $\approx -g_m \cdot R_d = -10^{-3} \cdot 10^3 \cdot 6 = -6$
- Then intrinsic gain  $\gg$  amplifier gain.

## AC analysis(gain vs frequency):

 


//comments:

- An AC analysis is done from 1hz to 1G hz .
- We out the  $v_{in} = 1$  then the gain equal the  $V_{out}$ .
- From the graph the DC gain is almost 6 then it meets the specs.

## 2nd: gain Non-linearity:


Vout vs Vin:

 

//comments:

- A DC analysis is made to sweep for the input voltage from 0 to VDD with a 2m V step size.
- Relation is not linear.
- It is obvious that the inverter characteristics that is present in any inverting stage.
- Then gain non-linearity is obvious.
- It starts quadratically with large  $V_{ds}$  then the device is saturated.
- Then  $V_{ds}$  starts to decrease gradually.
- Then device is in triode and acts as a resistor.
- Then gain expression is a function in  $V_{in}$ .


## Vout derivative vs Vin:

 

//comments:

- The Vout is sent to the calculator to get its derivative.
- It starts with no gain.
- Then nonlinear relation.
- In derive curve it appears that at first the gain increases as if it is linearly till it reaches a value near to the -6.5, then device goes in triode region.
- One of the problems of this technology is that the gain depends on the Vrd as Rd increases, I sacrifice with the swing, and I go to swing clipping occurs and goes to triode.

## Gm vs time:

 

//comments:

- the properties of the voltage source to apply a transient stimulus is set (sine wave of 1kHz frequency and 10mV amplitude superimposed on the DC input voltage).
- Then a transient analysis is done for 2 ms.
- It is obvious that gm varies with the input signal.
- Which means that this is a non linear relation.

//comments:

- The amplifier is not linear as gm varies with the input signal, and variation in input changes the bias points.